POOR MAN'S DAC

> analog Write () LM 358 10µF/10V