

INTERNAL OPAMP (only UND Rh WIFI)

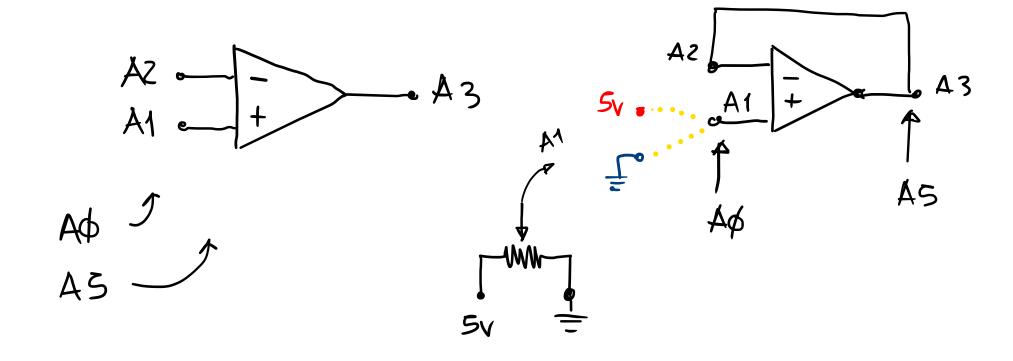

AMPLI NON INVERTENTE

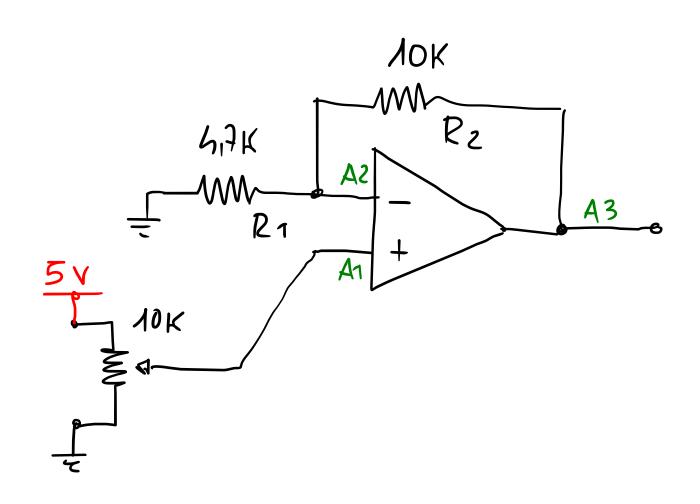

$$G = 1 + \frac{R_2}{R_1} = \frac{10}{5} = 3$$

COMPARATORE

