
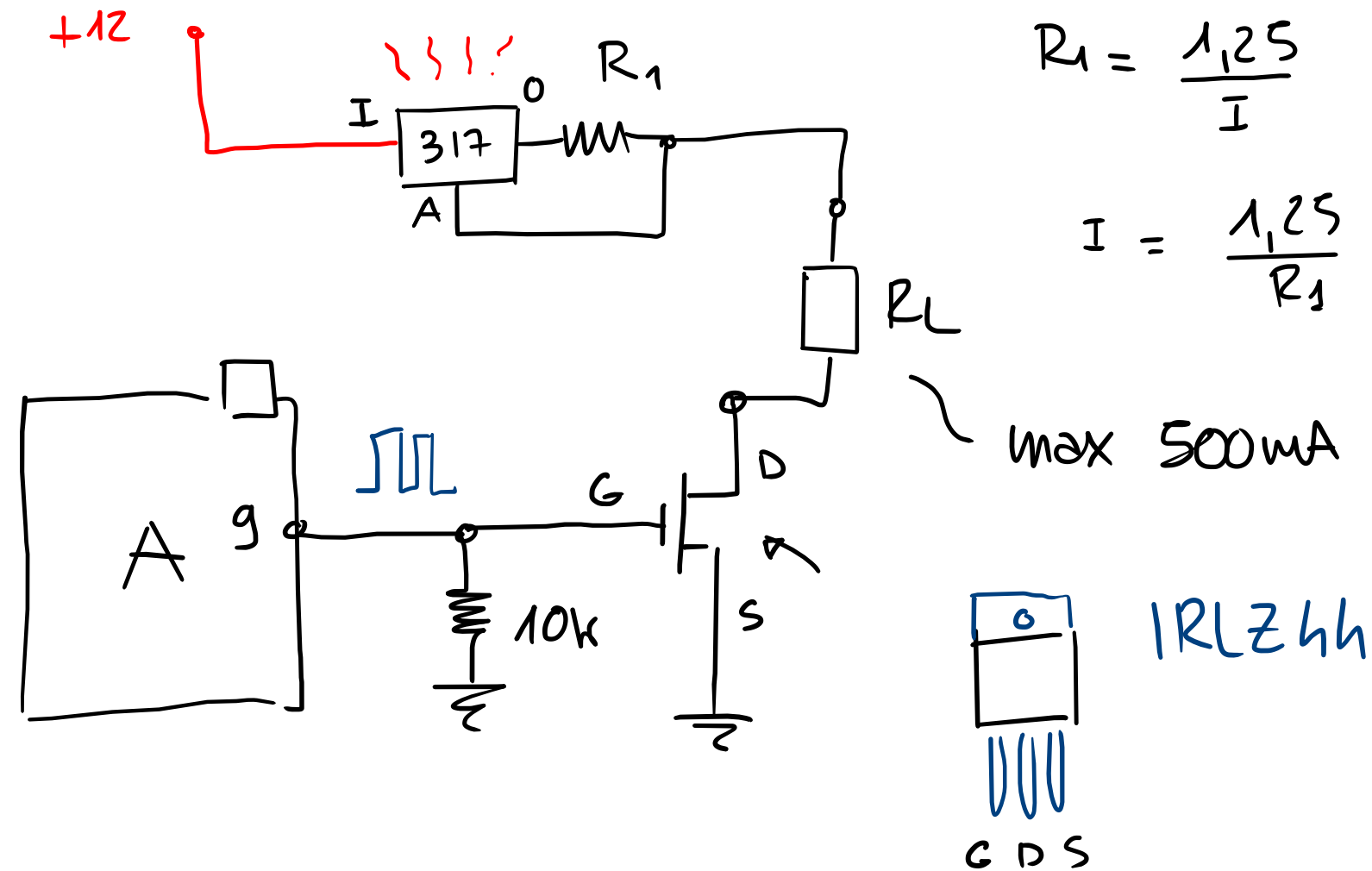


PWM LIMITATO IN CORRENTE

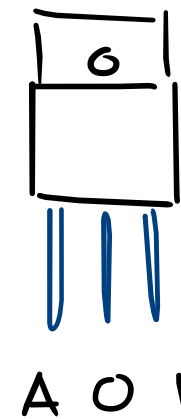

LM317



$$R_1 = \frac{1,25}{0,5} = 2,5 \Omega \leadsto 2,7 \Omega$$

$$P = i^2 R = 0,5^2 \cdot 2,7 = 0,6 \dots 0,7 \text{ W} \rightarrow \underline{2 \text{ W}}$$